

USN - 1MSISECO17

NAME - Anirudh Tiwari

SUBJECT - Field lines and Waves

SUBJECT CODE - EC43

CIE - 2

SEM - IV

PAGE - 9

SIGN - Anirudh

$$\Gamma = \frac{Z_L [Z_L - Z_0]}{(Z_L + Z_0) Z_L + Z_L^2 j\beta}$$

①

$$\Gamma = \frac{Z_L - Z_0}{(Z_L + Z_0) + 2Z_L j\beta}$$

$$|\Gamma| = \frac{1}{\sqrt{\frac{(Z_L + Z_0)^2}{(Z_L - Z_0)^2} + \frac{4Z_L^2 \beta^2}{(Z_L - Z_0)^2}}}$$

$$(Z_L + Z_0)^2 = (Z_L - Z_0)^2 + 4Z_L^2 \beta^2$$

$$\begin{aligned} \text{So, } \frac{(Z_L + Z_0)^2}{(Z_L - Z_0)^2} &= \frac{(Z_L - Z_0)^2 + 4Z_L^2 \beta^2}{(Z_L - Z_0)^2} \\ &= 1 + \frac{4Z_L^2 \beta^2}{(Z_L - Z_0)^2} \\ &= 1 + \frac{4Z_L^2}{(Z_L - Z_0)^2} \end{aligned}$$

$$|\Gamma| = \frac{1}{\sqrt{1 + \frac{4Z_L^2 \beta^2}{(Z_L - Z_0)^2}}}$$

$$\Theta = \frac{\pi}{2} \frac{A_0}{L}$$

Let max. threshold on reflection coefficient be where launch design for certain ranges of frequency must be done

$$Q_m = \cos^{-1} \left( \frac{(t_m) 2\sqrt{Z_L Z_0}}{\sqrt{1 - |t_m|^2} (Z_L - Z_0)} \right)$$

$$\frac{\Delta f}{f_0} = \frac{2 - 4 \cos^{-1} \left( \frac{|t_m|}{\sqrt{1 - |t_m|^2}} \frac{2\sqrt{Z_L Z_0}}{Z_L - Z_0} \right)}{\pi}$$

16.)  $SWR = 6$  ;  $V_{max}$  at  $0.721\lambda$

$Z_0 = 150\Omega$  ;  $l = 3.2\lambda$

Moving at  $0.721\lambda$  anti-clockwise

$|\Gamma| = 0.7$

$Z_L = 0.165 + j1.85$

i)  $Z_L = 24.75 + j27.75$

ii.)  $\Gamma_L = 0.7 \angle 158^\circ$

iii.)  $\Gamma_m = 0.7 \angle 87^\circ$

iv.) return loss = 3dB

v.) distance =  $(4 \times 0.5 + 0.475)\lambda$   
 $= 2.475\lambda$

36.)  $Z_L = (150 - j75)\Omega$   $Z_0 = 100$   $f = 1.5 \text{ GHz}$

SSSS

$d_1 = \lambda_2 - \lambda_{gk}$   
 $= 0.155 - 0.056$   
 $= (0.101)\lambda$

$d_1 = \lambda_1 - 0.25$   
 $= 0.398 - 0.25$   
 $= 0.148\lambda$

$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{1.5 \times 10^9} = 0.2 \text{ m}$

$d_1 = 0.101 \times 0.2$   
 $= 0.0202$

$d_1 = 0.148 \times 0.2$   
 $= 0.0296 \text{ m}$

1c.) Bandwidth performance of quarter wave line (QWL)  
 From definition impedance seen into junction of quarter wave line


$$Z_{in} = Z_1 \left[ \frac{Z_L + jZ_1 \tan \beta L}{Z_1 + jZ_L \tan \beta L} \right]$$

$$\text{when } \beta L = \frac{2\pi}{\lambda} \left( \frac{\lambda_0}{4} \right)$$

$$\text{when } \lambda = \lambda_0, \beta L = 0 = \frac{\pi}{2}$$

$$Z_1 = \sqrt{Z_0 Z_L}, \quad r = 0 = \text{reflection at junction.}$$

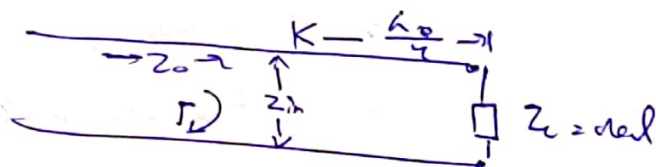If there is small change in operating freq. when  $f \neq f_0$  there is mismatch at junction result in reflection



$$T = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \quad \text{when } \lambda \neq \lambda_0 \text{ and } f \neq f_0$$

$$Z_{in} \neq Z_0$$

$$r = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$r = \frac{Z_1 \left[ \frac{Z_L + jZ_1 t}{Z_1 + jZ_L t} \right] - Z_0}{Z_1 \left[ \frac{Z_L + jZ_0 t}{Z_1 + jZ_L t} \right] + Z_0} \quad t = \tan \beta L$$

$$r = \frac{Z_1 Z_L + jZ_1^2 t - Z_0 Z_0 - Z_0 jZ_L t}{Z_1 Z_L + jZ_1^2 t + Z_0 Z_1 + jZ_0 Z_L t}$$

$$r = \frac{Z_1 [Z_L - Z_0] + j[Z_1^2 - Z_0^2] t}{Z_1 [Z_1 + Z_0] + j[Z_1^2 + Z_0^2] t}$$

$$\Gamma = \frac{Z_L(Z_L - Z_0)}{(Z_L + Z_0)Z_L + 2Z_L^2 j\beta}$$

③ ④

$$\Gamma = \frac{Z_L - Z_0}{(Z_L + Z_0) + 2Z_L j\beta}$$

$$|\Gamma| = \frac{1}{\sqrt{\frac{(Z_L + Z_0)^2}{(Z_L - Z_0)^2} + \frac{4Z_L^2}{(Z_L - Z_0)^2}}}$$

$$(Z_L + Z_0)^2 = (Z_L - Z_0)^2 + 4Z_L Z_0$$

$$\begin{aligned} \text{So, } \frac{(Z_L + Z_0)^2}{(Z_L - Z_0)^2} &= \frac{(Z_L - Z_0)^2 + 4Z_L Z_0}{(Z_L - Z_0)^2} \\ &= 1 + \frac{4Z_L Z_0}{(Z_L - Z_0)^2} \\ &= 1 + \frac{4Z_L^2}{(Z_L - Z_0)^2} \end{aligned}$$

$$|\Gamma| = \frac{1}{\sqrt{1 + \frac{4Z_L Z_0}{(Z_L - Z_0)^2} \sec^2 \alpha}}$$

$$\Theta = \frac{\pi}{2} \frac{A_0}{L}$$



Let max. threshold on reflection coefficient be 1 when launcher design for certain ranges of frequency must be done

$$\Theta_m = \cos^{-1} \left( \frac{(t_m) 2\sqrt{Z_L Z_0}}{\sqrt{1 - |t_m|^2} (Z_L - Z_0)} \right)$$


$$\frac{\Delta f}{f_0} = \frac{2 - 4 \cos^{-1} \left( \frac{|t_m| 2\sqrt{Z_L Z_0}}{\sqrt{1 - |t_m|^2} (Z_L - Z_0)} \right)}{\pi}$$



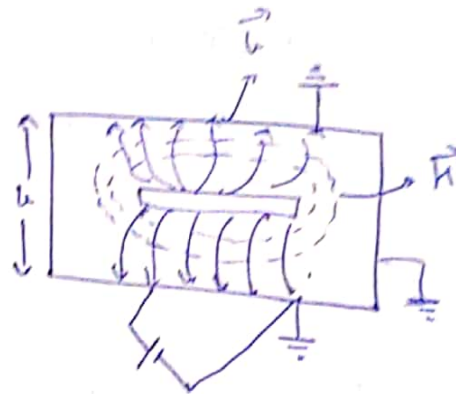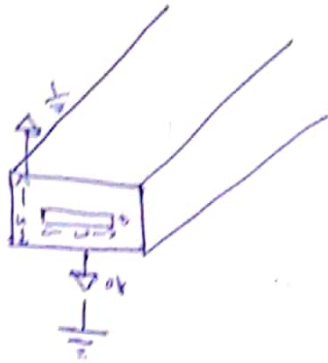① ②  
 (a) Strip line - Transmission line like two wire open line is bulky in size and costly. Hence miniaturized transmission lines are designed and they are called planar transmission where size is small so that it is used in Mmic.




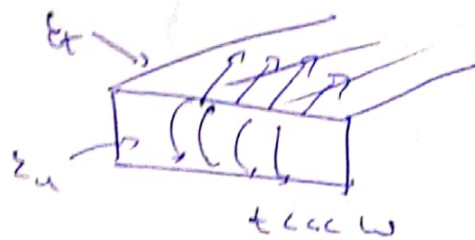Microstrip line - Microstrip line consists of a conductor strip of width  $w$  and thickness  $t$  such that  $t \ll w$  is mounted on a dielectric substrate of thickness  $h$  and permittivity  $\epsilon_r$ . When a signal propagates through the line, electric field emerges from the conductor strip and converges with magnetic field in circulation around the strip.



3c) Input impedance of lossless line

⑥

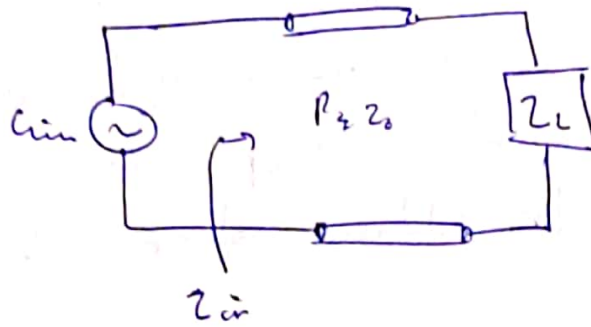

$$Z_{in} = \frac{V(z)}{I(z)} = \frac{V(-l)}{I(-l)} \quad (1)$$

wk.t

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

$$V(z) = V_0^+ (e^{-j\beta z} + \gamma e^{j\beta z}) = V_0^+ (e^{j\beta L} + \gamma e^{j\beta L})$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \gamma e^{j\beta z}) = \frac{V_0^+}{Z_0} (e^{j\beta L} - \gamma e^{j\beta L})$$

$$z = (-l)$$

$$Z_{in} = \frac{Z_0 (e^{j\beta L} + \gamma (e^{-j\beta L}))}{(e^{j\beta L} - \gamma e^{-j\beta L})}$$

$$= \frac{Z_0 (e^{j\beta L} + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-j\beta L})}{e^{j\beta L} - (\frac{Z_L - Z_0}{Z_L + Z_0}) e^{-j\beta L}}$$

$$= \frac{Z_0 \left[ (Z_L + Z_0) e^{j\beta L} + (Z_L - Z_0) e^{-j\beta L} \right]}{(Z_L + Z_0) e^{j\beta L} - (Z_L - Z_0) e^{-j\beta L}}$$

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta L}{Z_0 + jZ_L \tan \beta L} \right]$$

$$Z_{max} = \frac{V_{max}}{I_{min}} = \frac{|V_0^+| (1 + |\gamma|)}{|V_0^+| (1 - |\gamma|)} = Z_0 \frac{1 + |\gamma|}{1 - |\gamma|}$$

$$Z_{\min} = \frac{V_{\min}}{I_{\max}} = \frac{(V_0^+)(1 - |\gamma|)}{\frac{V_0^+}{Z_0}(1 + |\gamma|)} = Z_0 \frac{1 - |\gamma|}{1 + |\gamma|}$$


⑦

~~END~~



# Smith Chart


IMS19ECO17

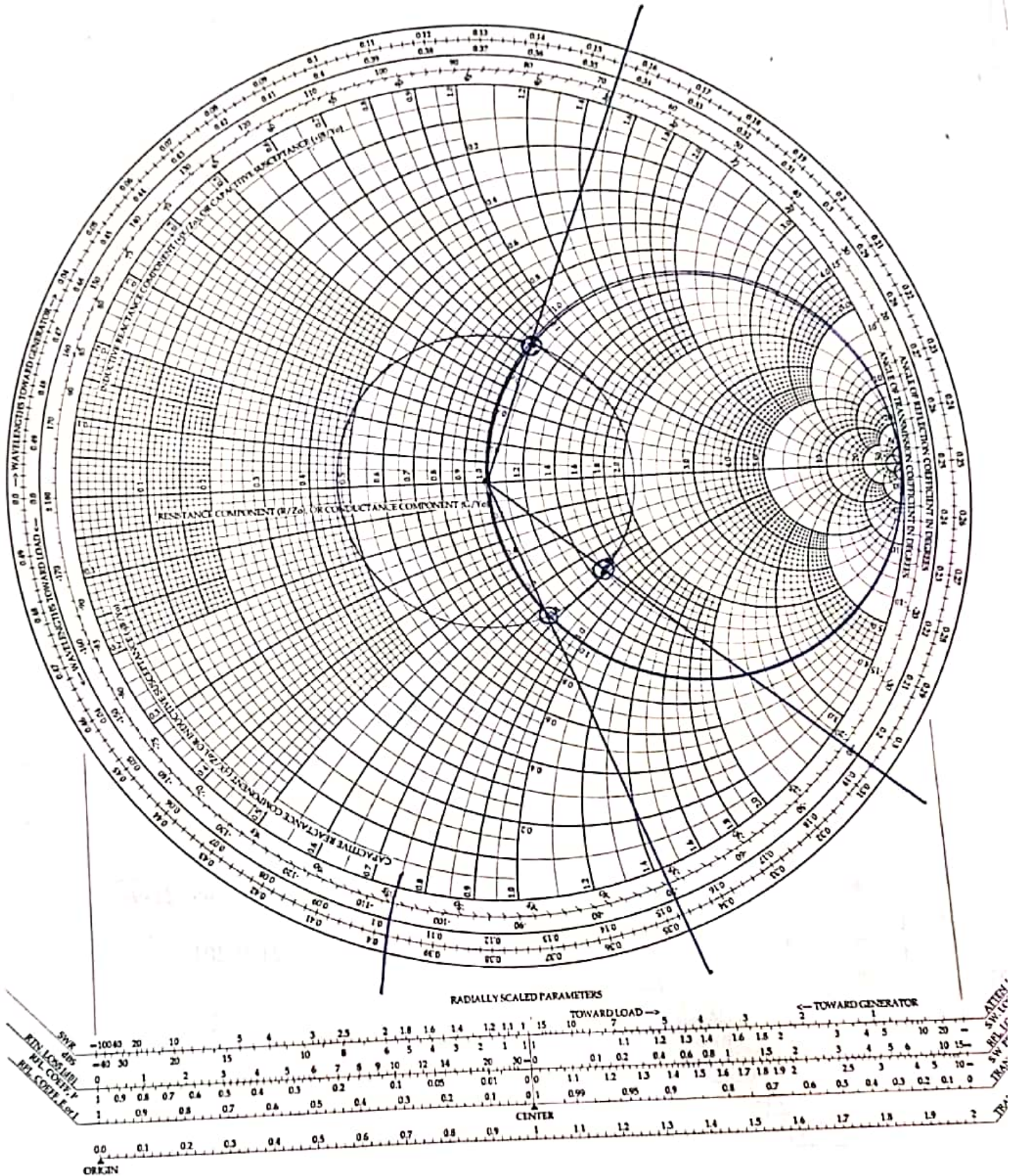



# Smith Chart

1MS19ECO17

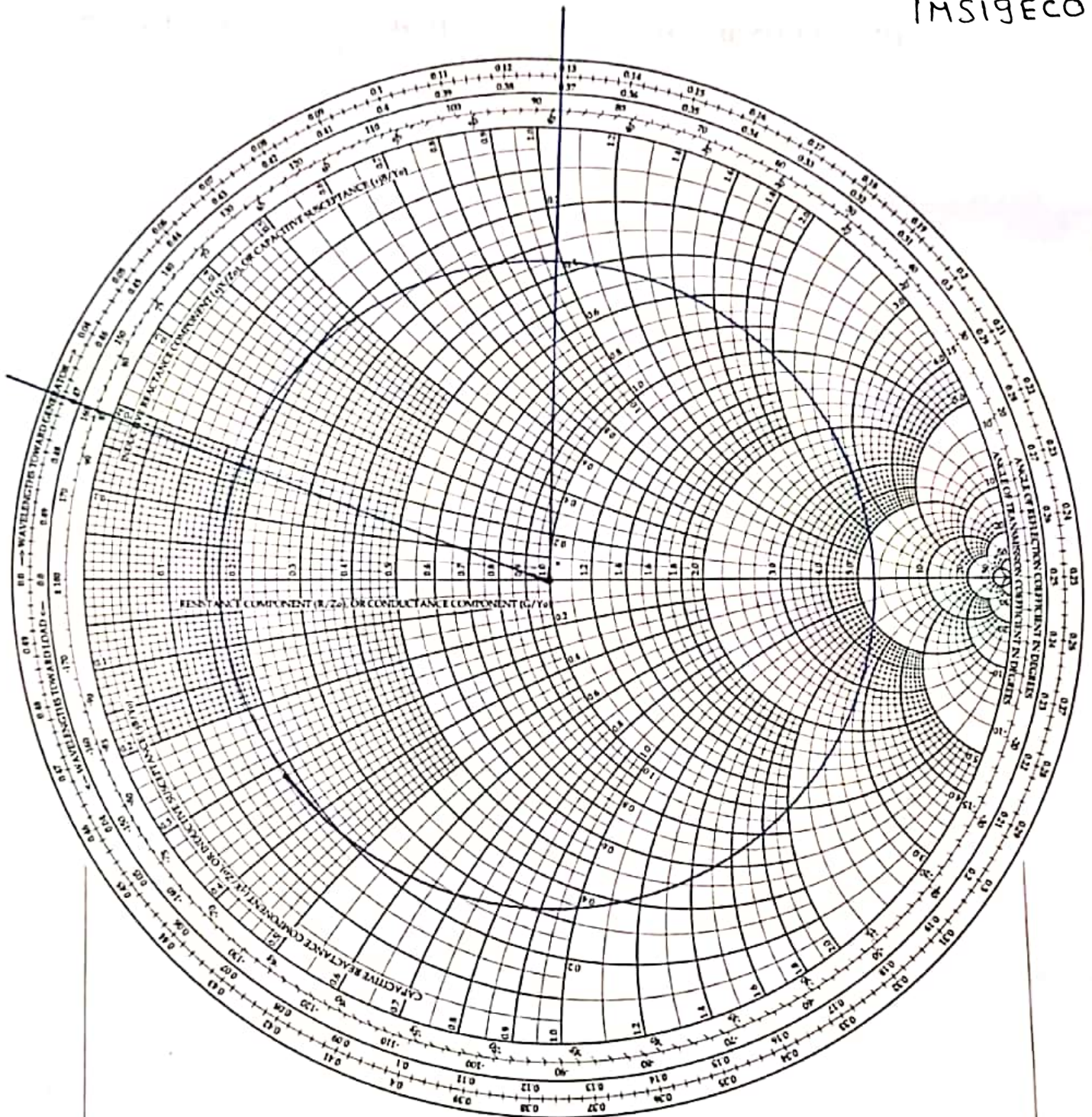

## RADIALLY SCALED PARAMETERS

